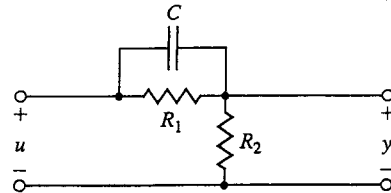


you would compute  $F$  and  $G$  for the standard state-variable description of the equations of motion.


- 2.9 Use node analysis to write the dynamic equations for the circuits shown in Fig. 2.40 and listed below:

- a) lead network
- b) lag network
- c) notch network


**FIGURE 2.40**  
Lead (a), lag (b) and  
notch (c) circuits



(a)

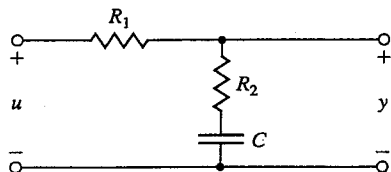

(b)

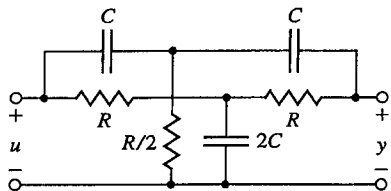

(c)



- 2.10 Using the step command in MATLAB, compare the response of each of the circuits in Problem 2.9 to a unit-step input. Assume  $R = R_1 = R_2 = 1 \Omega$  and  $C = 1 \text{ F}$ .

- 2.11 Use node analysis to write the dynamic equations for the op-amp circuits in Fig. 2.41 and listed below. Assume ideal operational amplifiers in every case.

- a) first-order op-amp lead network
- b) second-order op-amp circuit
- c) Sallen-Key circuit

- 2.12 Write the state equations for the electrical network shown in Fig. 2.42. Choose as state variables the capacitor voltage  $v_C$  and inductor current  $i_L$ .

## Problems for Section 2.6

- 2.29.** Figure 2.55 shows a simple pendulum system in which a cord is wrapped around a fixed cylinder. The motion of the system that results is described by the differential equation

$$(l + R\theta)\ddot{\theta} + g \sin \theta + R\dot{\theta}^2 = 0,$$


where

$l$  = length of the cord in the vertical (down) position,

$R$  = radius of the cylinder.

- (a) Write the state-variable equations for this system.  
 (b) Linearize the equation around the point  $\theta = 0$ , and show that for small values of  $\theta$  the system equation reduces to an equation for a simple pendulum, that is,

$$\ddot{\theta} + (g/l)\theta = 0.$$

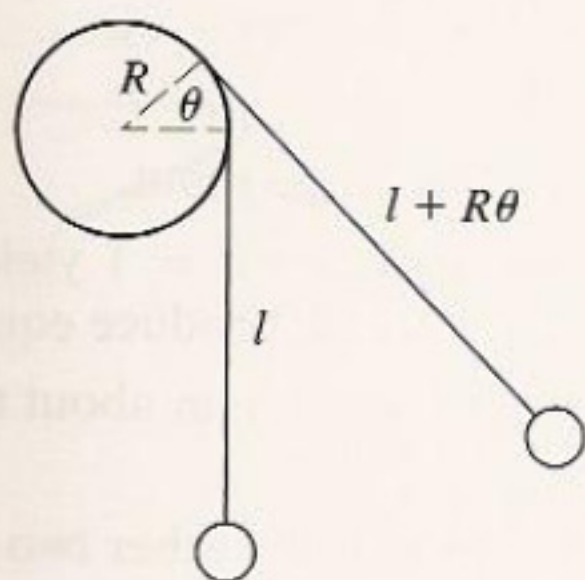

- 2.30.** A schematic for the satellite and scientific probe for the Gravity Probe-B (GP-B) experiment is sketched in Fig. 2.56. Assume that the mass of the spacecraft plus helium tank,  $m_1$ , is 2000 kg and that the mass of the probe,  $m_2$ , is 1000 kg. A rotor will float inside of the probe and will be forced to follow the probe with a capacitive forcing mechanism; however, this will have no effect on  $m_2$ . The spring constant of the coupling,  $k$ , is  $3.2 \times 10^6$ . The viscous damping,  $b$ , is  $4.6 \times 10^3$ .

- (a) Write the equations of motion for the system consisting of masses  $m_1$  and  $m_2$  using the inertial position variables,  $y_1$  and  $y_2$ .  
 (b) The actual disturbance,  $u$ , is a micrometerorite and the resulting motion is very small. Therefore, rewrite your equations with the scaled variables  $z_1 = \frac{y_1}{10^6}$ ,  $z_2 = \frac{y_2}{10^6}$ , and  $v = 1000u$ .  
 (c) Put the equations in state-variable form using the state  $\mathbf{x} = [z_1 \ \dot{z}_1 \ z_2 \ \dot{z}_2]^T$ , the output  $y = z_2$ , and the input an impulse,  $u = 10^{-3}\delta(t)$  N·sec on mass  $m_1$ .  
 (d) Using the numerical values, enter the equations of motion into MATLAB in the form


$$\dot{\mathbf{x}} = \mathbf{F}\mathbf{x} + \mathbf{G}u, \quad (2.131)$$

$$y = \mathbf{H}\mathbf{x} + Ju \quad (2.132)$$



**Figure 2.56**

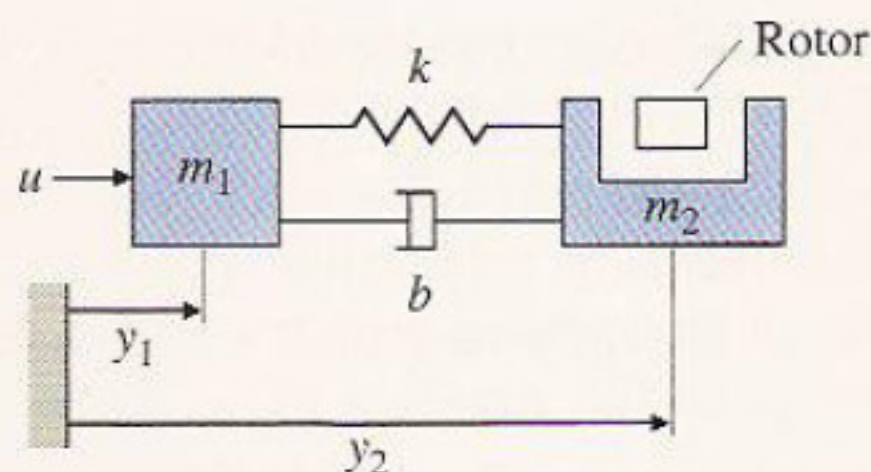Schematic diagram of the GP-B satellite and probe



and define the MATLAB system:  $\text{sysGPB} = \text{ss}(F, G, H, J)$ . Plot the response of  $y$  caused by the impulse with the MATLAB command  $\text{impz}(\text{sysGPB})$ . This is the signal the rotor must follow.

- 2.31.** The circuit shown in Fig. 2.57 has a nonlinear conductance  $G$  such that  $i_G = g(v_G) = v_G(v_G - 1)(v_G - 4)$ . The state differential equations are

$$\frac{di}{dt} = -i + v,$$


$$\frac{dv}{dt} = -i + g(u - v),$$

where  $i$  and  $v$  are the states and  $u$  is the input.

- One equilibrium state occurs when  $u = 1$  yielding  $i_1 = v_1 = 0$ . Find the other two pairs of  $v$  and  $i$  that will produce equilibrium.
- Find the linearized model of the system about the equilibrium point  $u = 1$ ,  $i = v_1 = 0$ .
- Find the linearized models about the other two equilibrium points.

**Figure 2.57**

Nonlinear circuit for Problem 2.31

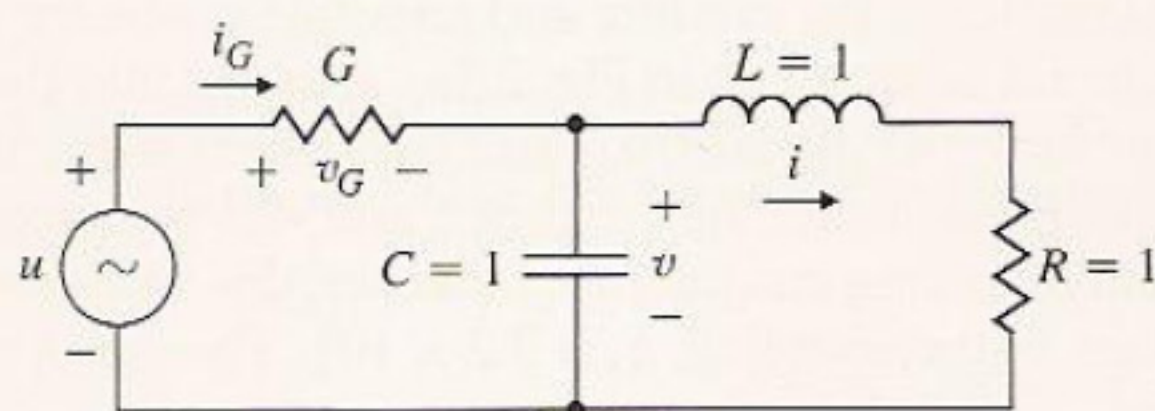

- 2.32.** Consider the circuit shown in Fig. 2.58;  $u_1$  and  $u_2$  are voltage and current sources, respectively, and  $R_1$  and  $R_2$  are nonlinear resistors with the following characteristics:

$$\text{Resistor 1 : } i_1 = G(v_1) = v_1^3,$$

$$\text{Resistor 2 : } v_2 = r(i_2),$$

where the function  $r$  is defined in Fig. 2.59.

- Show that the circuit equations can be written as

$$\dot{x}_1 = G(u_1 - x_1) + u_2 - x_3$$

$$\dot{x}_2 = x_3$$

$$\dot{x}_3 = x_1 - x_2 - r(x_3).$$